

Lecture 5


Digital Design with FPGA

Peter Cheung
Department of Electrical & Electronic Engineering
Imperial College London

Course webpage: www.ee.ic.ac.uk/pcheung/teaching/EE2_CAS/
E-mail: p.cheung@imperial.ac.uk

How to describe/specify digital circuits?

Schematic diagram
& gates

 

Boolean equation

$$\text{out6} = \neg \text{in3} * \neg \text{in2} * \neg \text{in1} + \text{in3} * \text{in2} * \neg \text{in1} * \neg \text{in0} + \neg \text{in3} * \text{in2} * \text{in1} * \text{in0}$$

Truth table

in[3..0]	out[6:0]
0000	1000000
0001	1111001
0010	0100100
0011	0110000
0100	0011001
0101	0010010
0110	0000010
0111	1111000
1000	0000000
1001	0010000

Hardware Description Language
(HDL)


3-to-1 MUX

```

module mux32three(i0,i1,i2,sel,out);
input [31:0] i0,i1,i2;
input [1:0] sel;
output [31:0] out;
reg [31:0] out;


always @ (i0 or i1 or i2 or sel)
begin
    case (sel)
        2'b00: out = i0;
        2'b01: out = i1;
        2'b10: out = i2;
        default: out = 32'bx;
    endcase
end
endmodule
    
```

Timing Diagram

 


Basic digital building blocks


Primitive Logic Gates

 


Multiplexers

 

Arithmetic circuits

 


Encoders

 


Inputs								Outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	Q ₂	Q ₁	Q ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	x	0	0	1
0	0	0	0	0	1	x	x	0	1	0
0	0	0	0	1	x	x	x	0	1	1
0	0	0	1	x	x	x	x	1	0	0
0	0	1	x	x	x	x	x	1	0	1
0	1	x	x	x	x	x	x	1	1	0
1	x	x	x	x	x	x	x	1	1	1



Flipflops and Registers

 

Decoders

 

Cause & Effect

  

Input B going high **causes** X to go low

Input A going low **causes** X to go high

Propagation Delay:


The time delay between a cause (an input changing) and its effect (an output changing), assuming output load capacitance of 30pF.

Example: 74AC00: Advanced CMOS 2-input NAND gate

	min	typ	max	
$A \uparrow$ to $X \downarrow$ (t_{PHL})	1.5	4.5	6.5	ns
$A \downarrow$ to $X \uparrow$ (t_{PLH})	1.5	6.0	8.0	ns

t_{PHL} and t_{PLH} refer to the direction that the output changes:
high-to-low or low-to-high.

D-Flipflop (1)

 

Notation:


- > input effect happens on the rising edge
- C1 C $\Rightarrow$ Clock input, 1 $\Rightarrow$ This input is input number 1.
- 1D D $\Rightarrow$ Data input,
1 $\Rightarrow$ This input is controlled by input number 1.

The meaning of a number depends on its position:

A number after a letter is used to identify a particular input.

A number before a letter means that this input is controlled by one of the other inputs.


D-Flipflop (2)

 

Cause and Effect:

- CLOCK $\uparrow$ causes Q to change after a short delay. This is the only time Q ever changes.
- The value of D just before CLOCK $\uparrow$ is the new Q.
- Propagation delay CLOCK $\uparrow$ to Q is typically 1 ns.
- Propagation delay DATA to Q **does not make sense** since DATA changing does not cause Q to change.


Ripple Counter

 


- Notice inverters on the CLOCK and DATA inputs
- Least significant bit of a number is always labelled 0

Propagation Delay: CLOCK↓ to Q2 = $3 \times 1\text{ns} = 3\text{ns}$

 State Diagram
(not including transient states):




Synchronous Counter

 



The logic block must add 1 onto the current value of the counter, Q , to generate the next value of the counter, D . Suppose it has a propagation delay of 1ns.

 - A register is a bunch of flipflops with the same CLOCK.
- The individual flipflops are rectangles stacked on top of each other. Only the top one is labelled.
- All shared signals (e.g. the CLOCK input) go to the notched common control block at the top of the stack.



All flipflops change state within a fraction of nanosecond of each other.

  
Old ways of implementing digital circuits



- ◆ Discrete logic – based on gates or small packages containing small digital building blocks (at most a 1-bit adder)
- ◆ De Morgan's theorem – theoretically we only need 2-input NAND or NOR gates to build anything
- ◆ Tedious, expensive, slow, prone to wiring errors



 
Early integrated circuits based on gate arrays



- ◆ Rows of gates – often identical in structure
- ◆ Connected to form customer specific circuits
- ◆ Can be full-custom (i.e. completely fabricated from scratch for a given design)
- ◆ Can be semi-custom (i.e. customisation on the metal layers only)
- ◆ Once fabricated, the design is fixed


Modern digital design – full custom IC

 - ◆ Intel Core i7
- ◆ $> \frac{3}{4}$ billion trans.
- ◆ Very expensive to design
- ◆ Very expensive to manufacture
- ◆ Not viable unless the market is very large




Field Programmable Gate Arrays (FPGAs)

- ◆ Combining idea from Programmable Logic Devices (PLDs – Yr 1 Lecture 8) and gate arrays
- ◆ First introduced by Xilinx in 1985
- ◆ Arrays of logic blocks (to implement logic functions)
- ◆ Lots of programmable wiring in routing channels
- ◆ Very flexible I/O interfacing logic core to outside world
- ◆ Two dominant FPGA makers:
 - Xilinx and Altera
- ◆ Other specialist makers e.g. Actel and Lattice Logic

 


Configurable Logic Block (or Logic Element)

 - ◆ Based around Look-up Tables (LUTs), most common with 4-inputs
- ◆ Optional D-flipflop at the output of the LUT
- ◆ 4-input LUT can implement ANY 4-input Boolean equation (truth-table)
- ◆ Special circuits for cascading logic blocks (e.g. carry-chain of a binary adder)





Logic Element
(LE)

 

- ◆ Each logic block has pins located for easy access:


Programmable Routing

  - ◆ Between rows and columns of logic blocks are wiring channels
- ◆ These are programmable – a logic block pin can be connected to one of many wiring tracks through a programmable switch
- ◆ Xilinx FPGAs have dedicated switch block circuits for routing (more flexible)
- ◆ Each wire segment can be connected in one of many ways:




The Idea of Configuring the FPGA

- ◆ Programming an FPGA is NOT the same as programming a microprocessor
- ◆ We download a **BITSTREAM** (not a program) to an FPGA
- ◆ Programming an FPGA is known as **CONFIGURATION**
- ◆ All LUTs are configured using the BITSTREAM so that they contain the correct values to implement the Boolean logic
- ◆ Shown here is a typical implementation of a 4-LUT circuit
 - ABCD are the FOUR inputs
 - There are four levels of 2-to-1 multiplexer circuits
 - The 16-inputs to the mux tree determine the Boolean function to be implemented as in a truth-table
 - These 16 binary values are stored in registers (DFF)
 - Configuration = setting the 16 registers to 1 or 0

 


Configuring the **routing** in an FPGA

 - ◆ At each interconnect site, there is a transistor switch which is default OFF (not conducting)
- ◆ Each switch is controlled by the output of a 1-bit configuration register
- ◆ Configuring the routing is simply to put a '1' or '0' in this register to control the routing switches
- ◆ Bitstream is either stored on local flash memory or download via a computer
- ◆ Configuration happens on power-up




Max 10 FPGA – chip level view

 


- ❖ Intel/Altera's Max 10 FPGA
- ❖ Low cost family
- ❖ Inside FPGA, it has:
 - Logic Array Blocks (LABs) containing Logic Elements (LEs)
 - Embedded Memory Blocks
 - Embedded Multiplier Blocks
 - Clock Blocks
 - Internal Flash (program/data)
 - Configurable I/O circuits
 - Phase-locked Loops (PLL)
 - Analog-to-Digital converter Block

Max 10 FPGA Logic Element

 


- ❖ Intel/Altera's Max 10 FPGA
- ❖ Device is 10M50DAF484C7G
- ❖ 50,000 Logic Elements (LEs)
- ❖ Classical 4-LUT with D-FF
- ❖ Two dedicated paths between LEs:
 - Carry chain
 - Register cascade chain

Max 10 Logic Array Block (LAB)

 

- ❖ Logic Element (LE)
 - 4 LUT
 - Register
 - Output routing logic
- ❖ Logic Array Block
 - 16 Logic Elements
 - Local Lab Control
 - Routing inside LAB

Design Tools – Quartus Prime Lite

 

- ◆ Quartus Prime Lite – a comprehensive design tools for Intel/Altera FPGAs
- ◆ Special web edition free to download from (need registration):
 - <https://fpgasoftware.intel.com/18.0/?edition=lite&platform=windows>
 - Features include (see introduction to Quartus II):
 - design entry
 - compilation from Hardware Description Languages (HDL)
 - synthesis
 - simulation
 - timing analysis
 - power analysis
 - project management

DE10-Lite FPGA Board

