

EE2 Circuits and Systems



Revision Lecture

Lab 1 & 2 Explained

Prof Peter Y. K. Cheung
Imperial College London

URL: www.ee.ic.ac.uk/pcheung/teaching/EE2_CAS/
E-mail: p.cheung@imperial.ac.uk

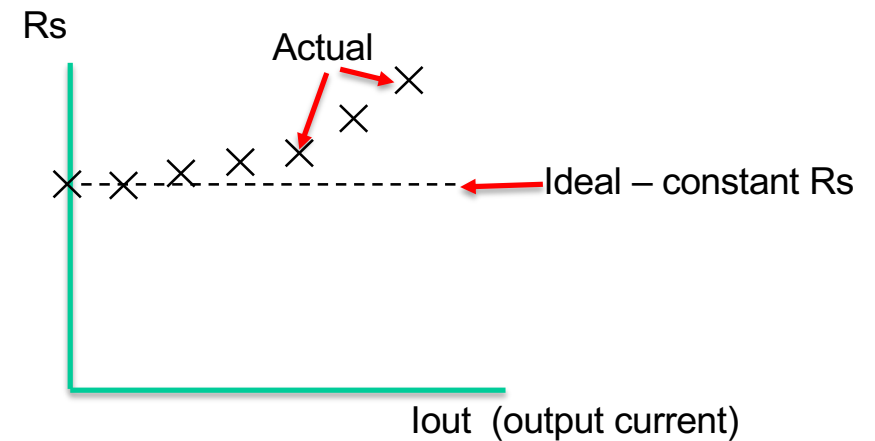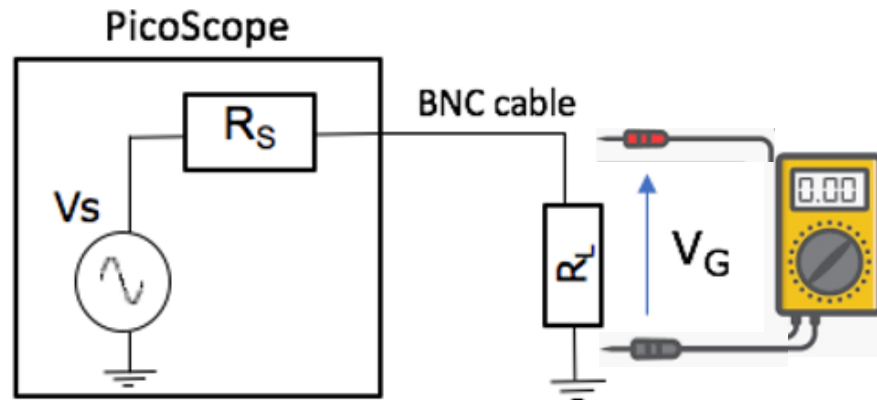
Task 1 – Output impedance of PicoScope SigGen



R_L	220	470	1k	10k	100k	∞
V_G (mV)						
R_s						


Task 2 – Using a Unity Gain Amplifier (2)

- ◆ Add R3 (200k) – makes no difference, but ready for Task 3

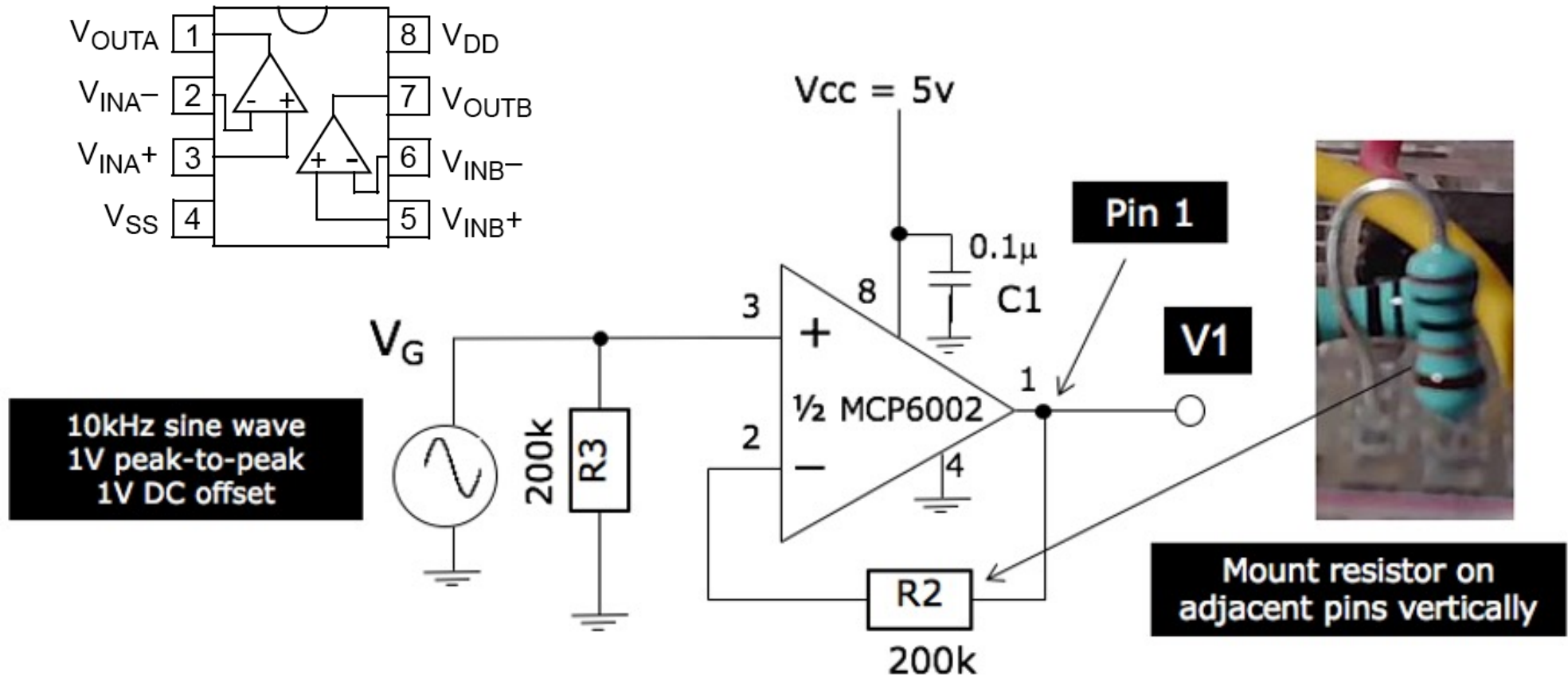


Task 3 – x4 Amplifier Failure (1)

- ◆ Add R4. The gain of the amplifier should be x4.
- ◆ However, you will see that V_1 shows a sine wave with top of it “clipped”.

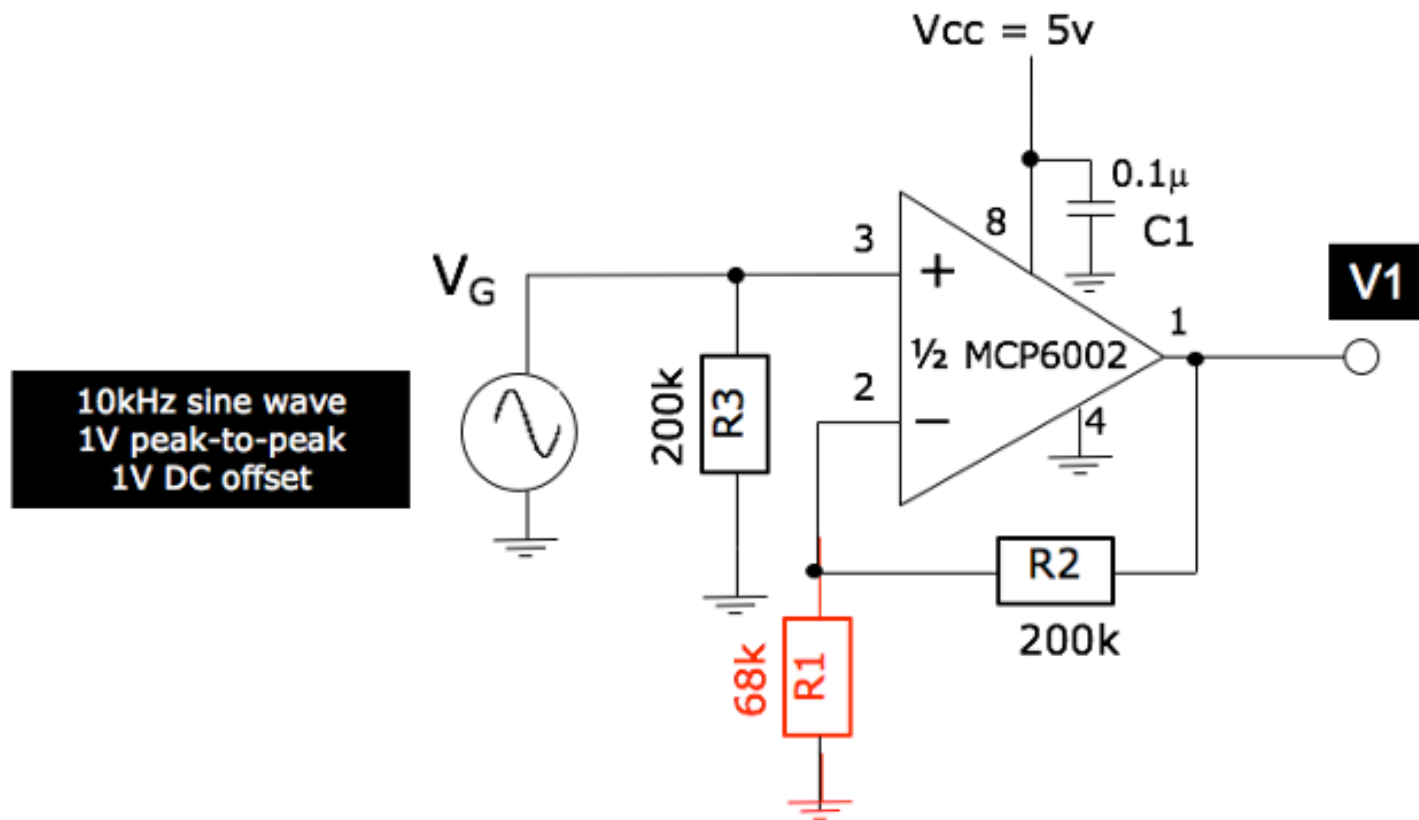


Task 3 – x4 Amplifier Success (1)

- ◆ Add C2 and C3. This will now work. Why?

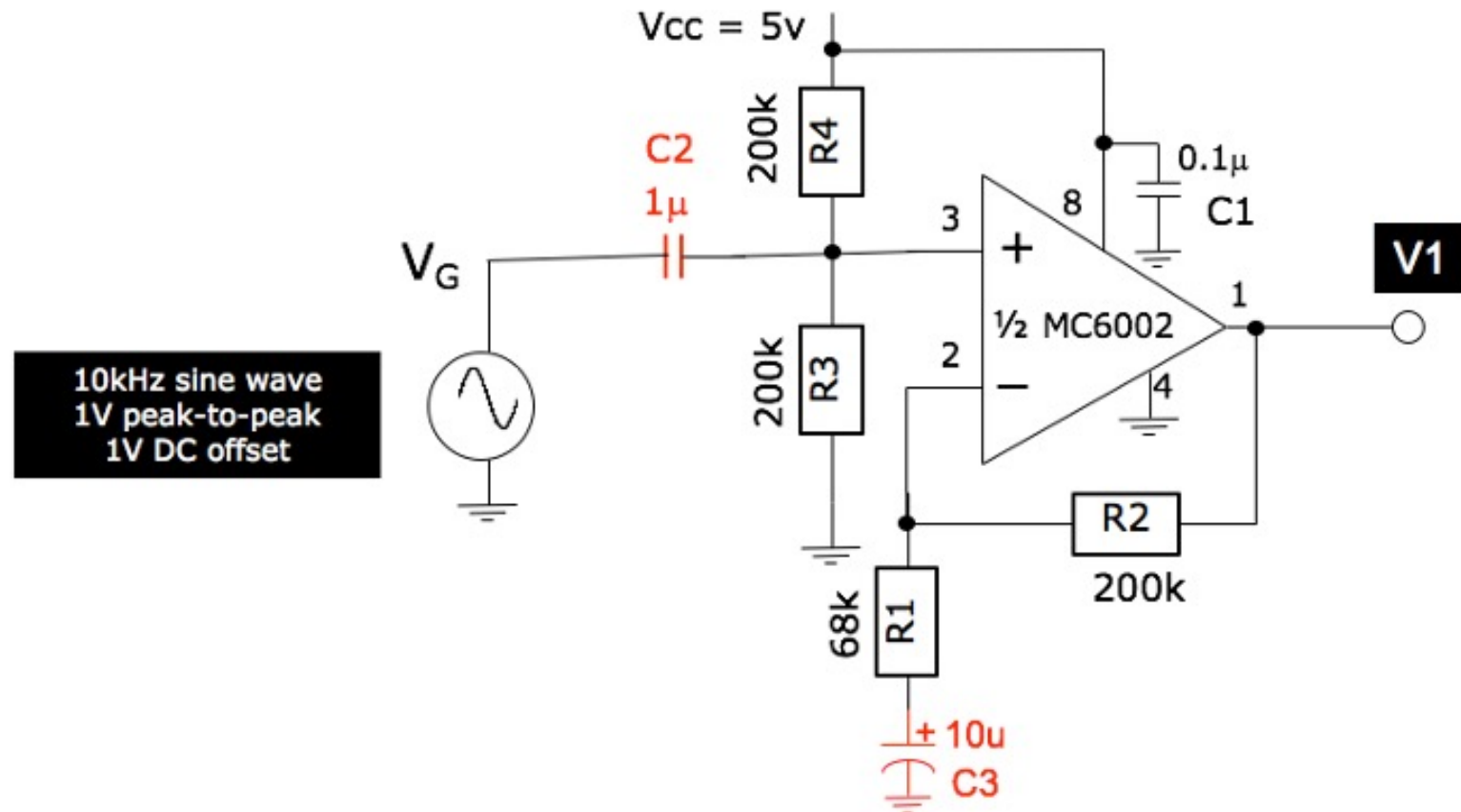


Task 3 – x4 Amplifier Success (2)

- ◆ Consider what happens at DC source (principle of superposition):
 1. C2 is open-circuit, so 2.5V dc is blocked by C2. Instead, V+ is now at 2.5V because of R1 and R2 (voltage divider).
 2. C3 is open-circuit. Therefore the op-amp is now a x1 amplifier as in Task 2.

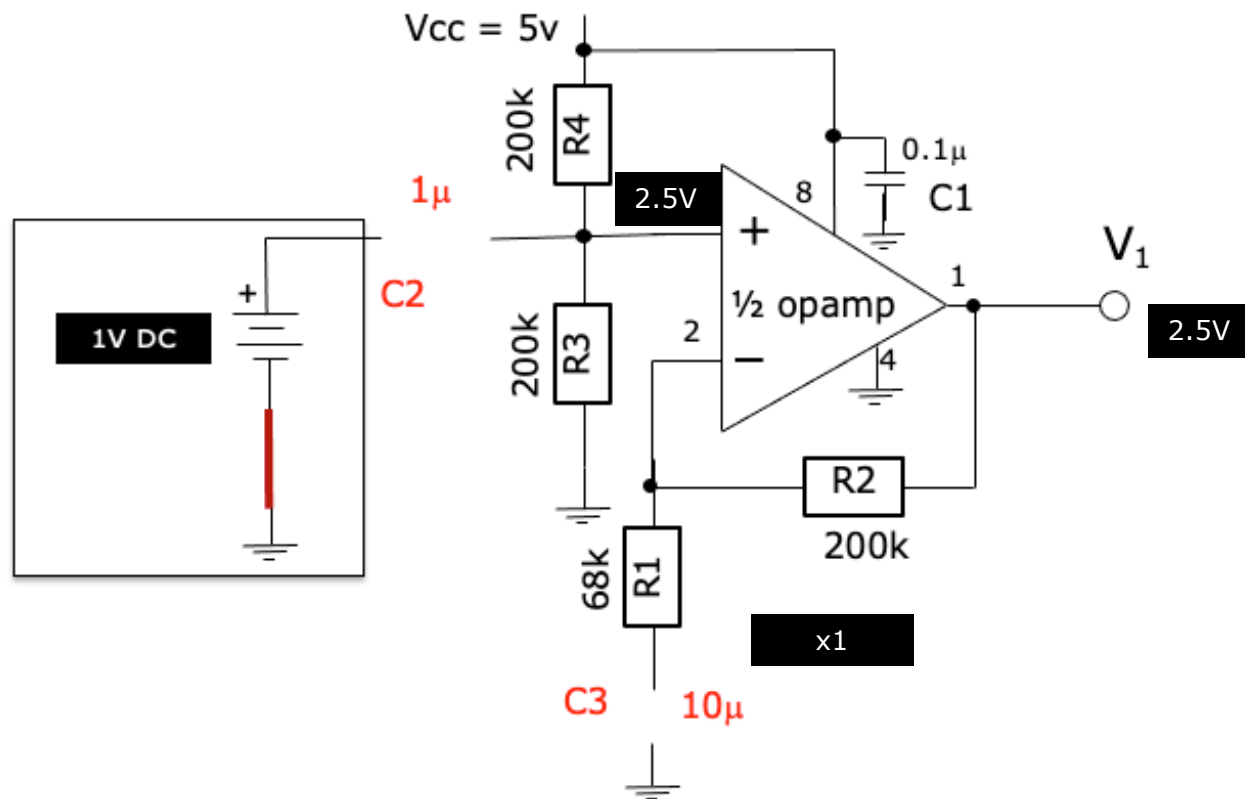


Task 3 – x4 Amplifier Success (3)

- ◆ Consider what happens at high frequency (e.g. 10kHz sine wave):
 1. C2 is short-circuit, so V_G goes directly to V_+ .
 2. C3 is short-circuit. Therefore the op-amp is now a x4 amplifier

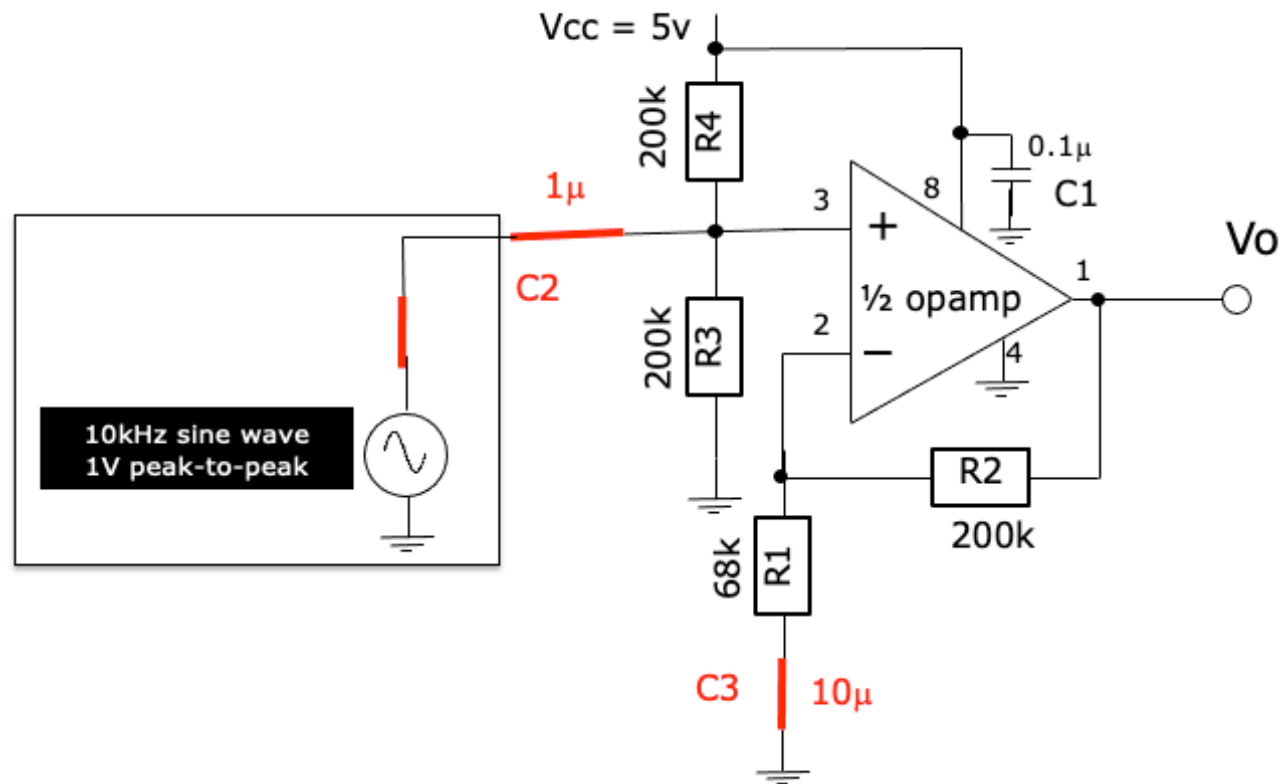

Task 4 – Better bias circuit (1)

- ◆ Bias voltage at pin 3 is poor because

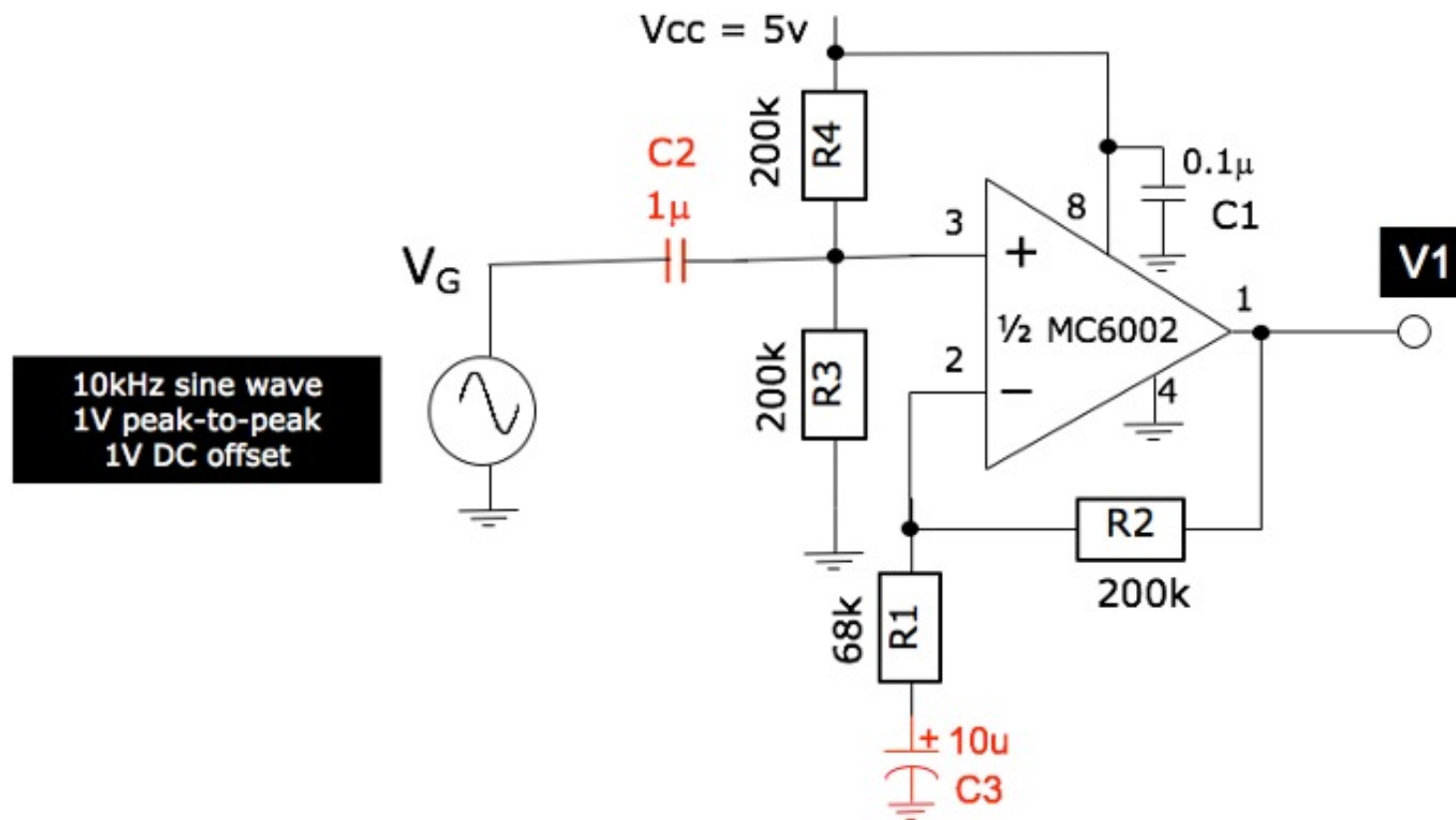


Task 4 – Better bias circuit (2)

- ◆ Replace resistor divider bias circuit with proper voltage reference


Why is R3 necessary?

What is the loading seen by the PicoScope signal generator?

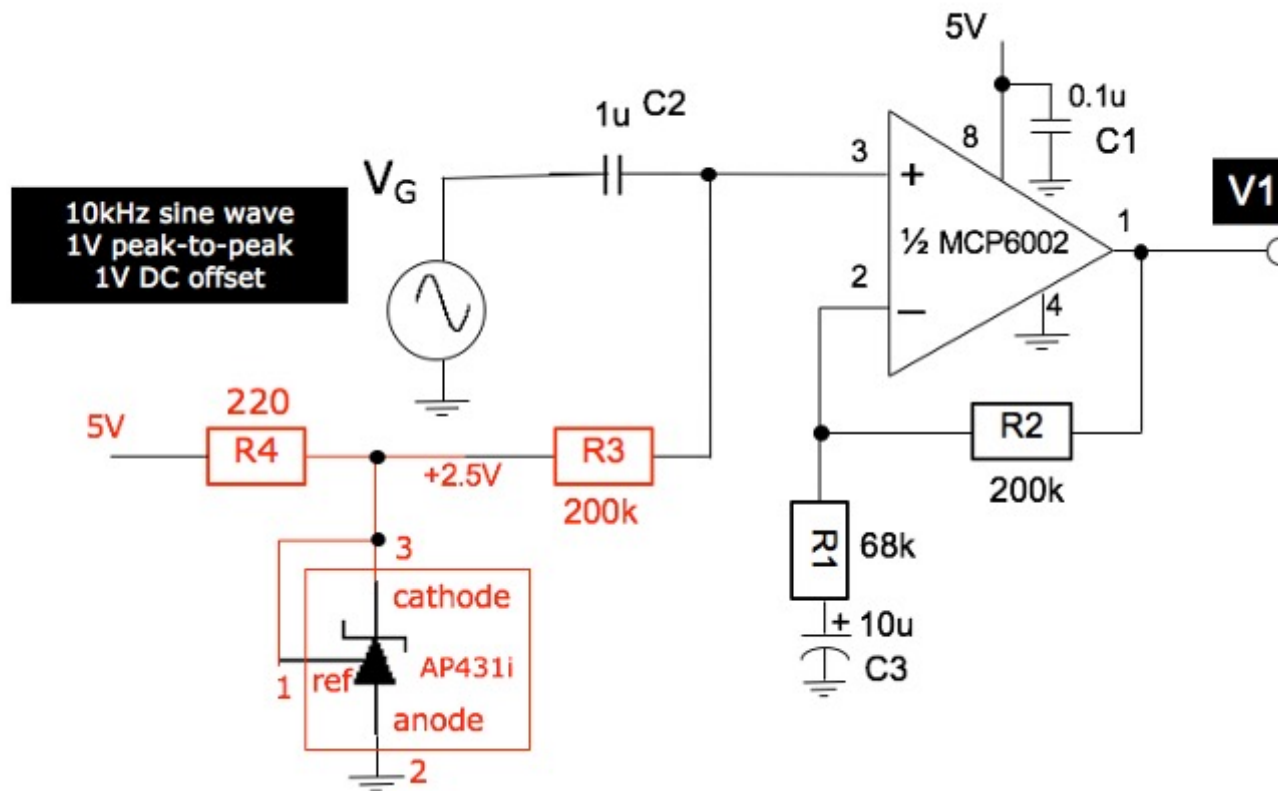


Task 5 – Large Gain amplifier failure

- ◆ Replace R1 with 2k ohm resistor. Gain = $1 + R2/R1 = 101$

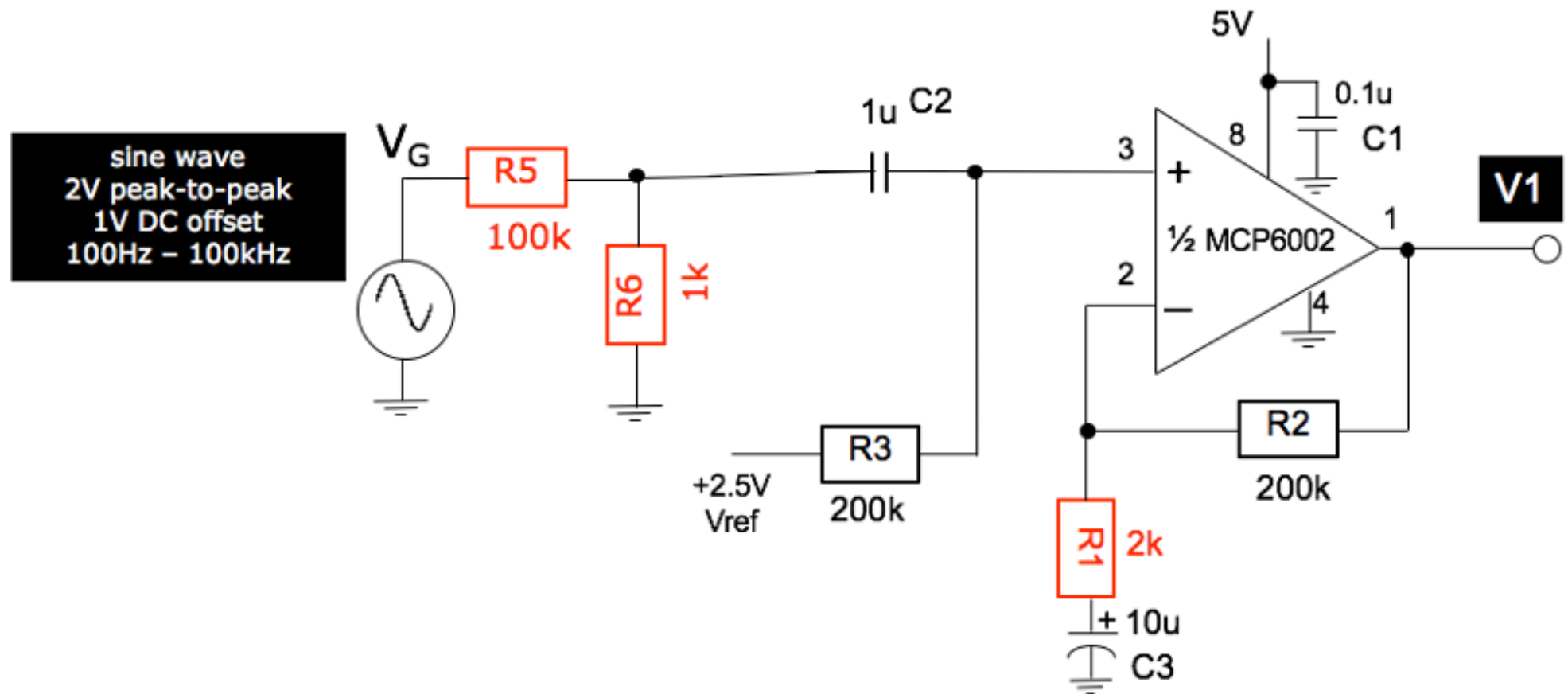


Task 5 – Gain-Bandwidth Product limit

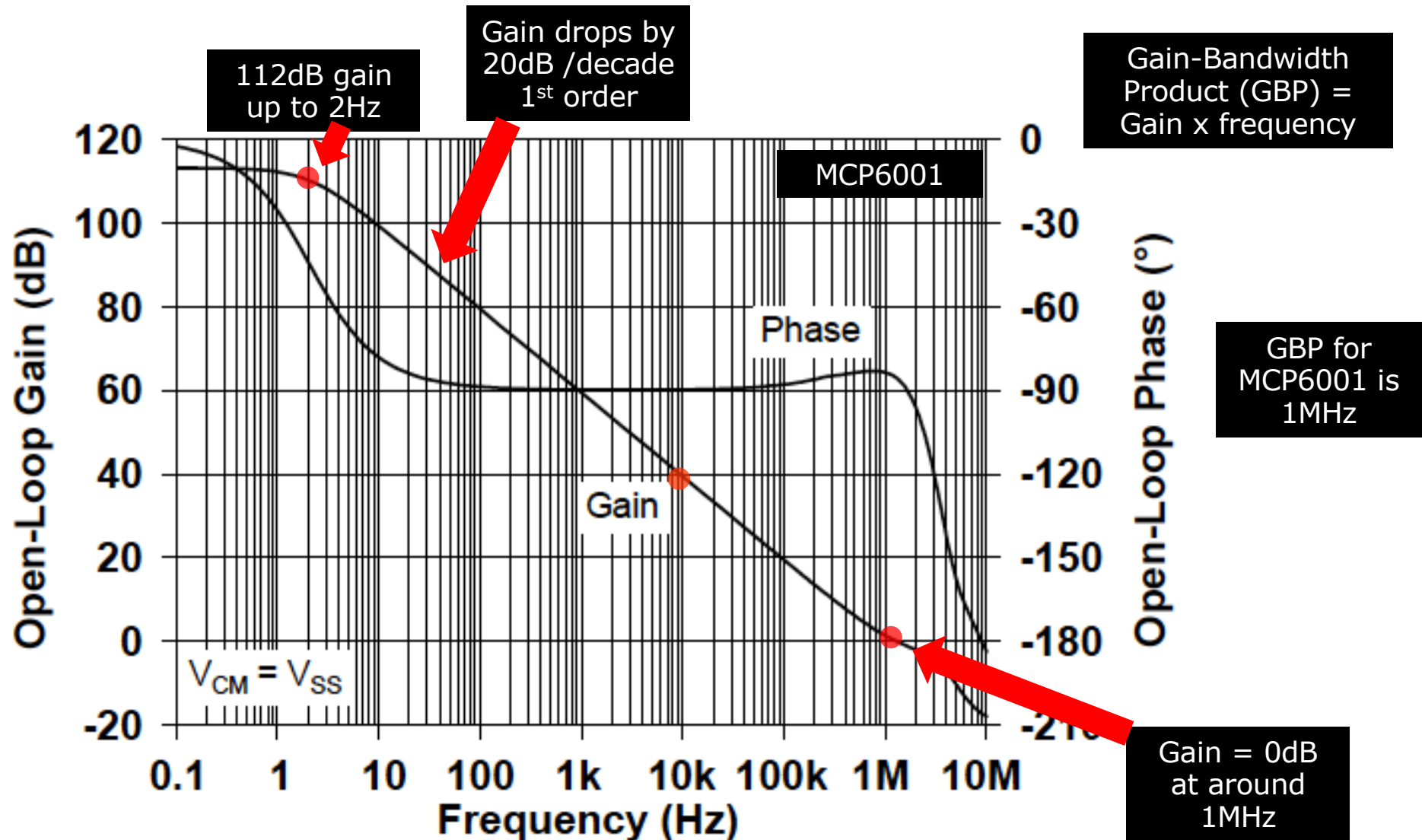


Task 6 – High gain amplifier in 2 stages (1)

- ◆ Stage 1: non-inverting amplifier with GAIN = 21
- ◆ Replace R1 with a 10k ohm resistor. Now gain is x21

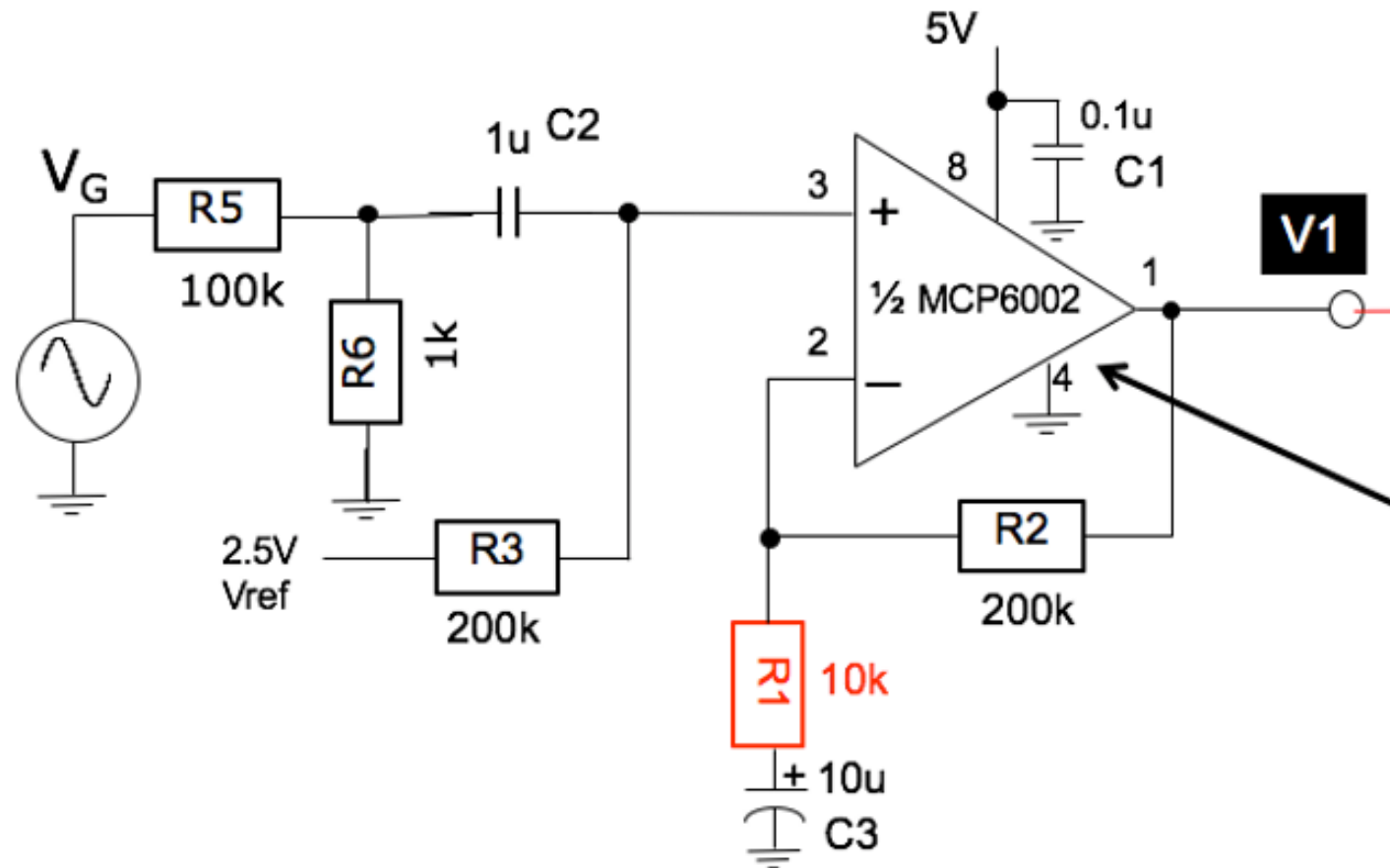

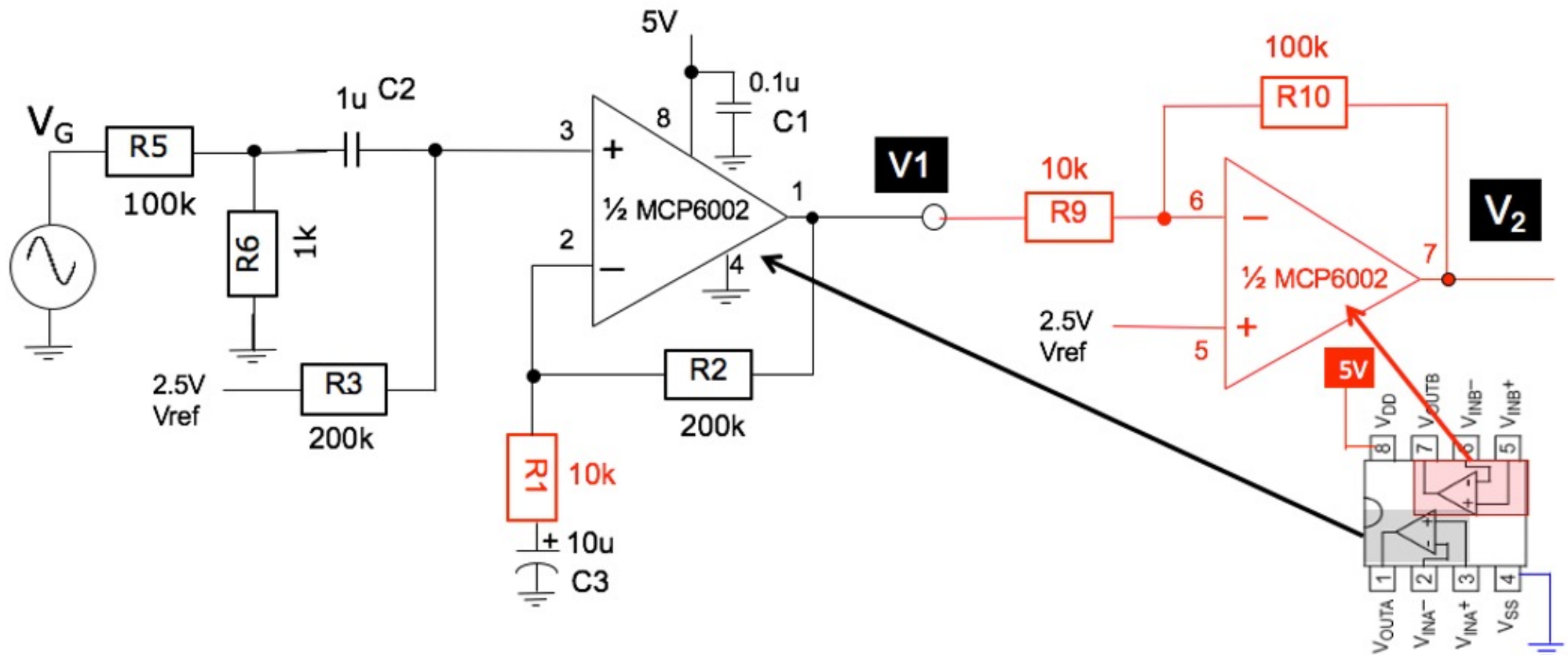Task 6 – x210 amplifier in 2 stages (2)


- ◆ Stage 2: inverting amplifier with GAIN = -10 (circuit in RED)
- ◆ Now check Vo1 and Vo2



Topic 11 slide 8

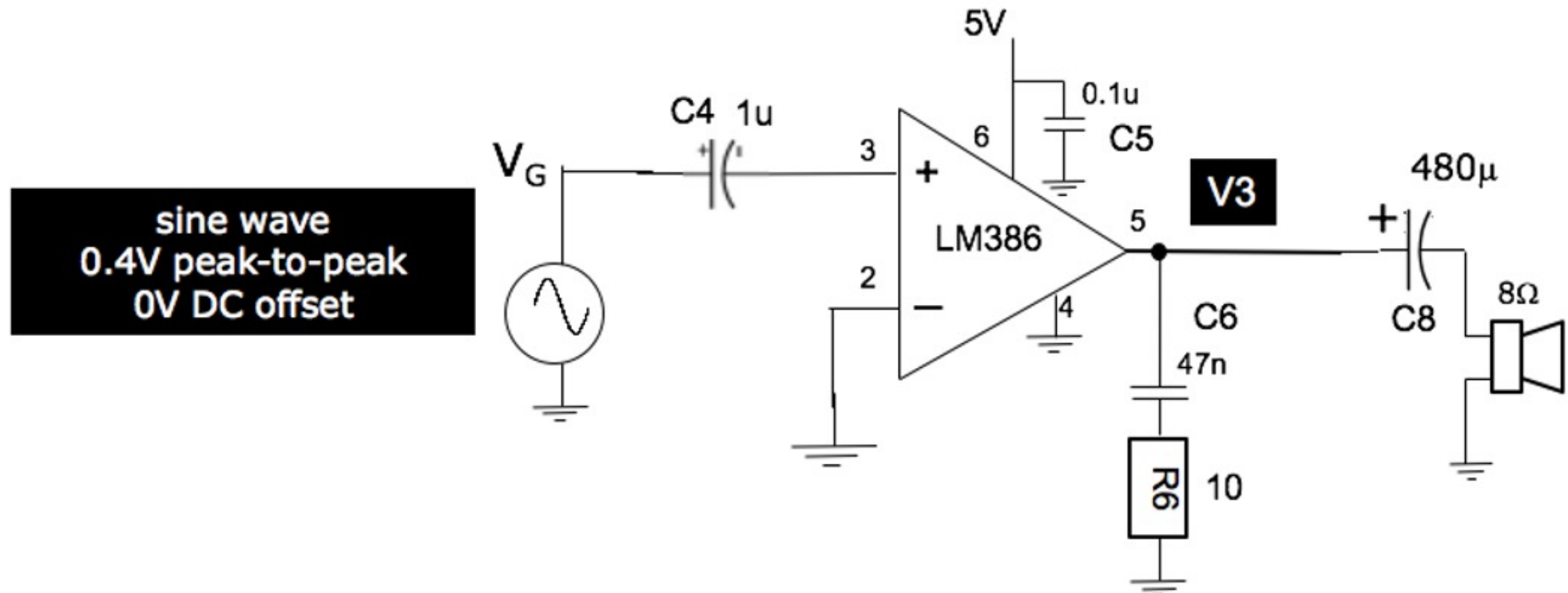
Task 7 – Audio Amplifier for 8 ohm speaker

- ◆ Op-amp only can only deliver at most 20mA current at its output
- ◆ Need special amplifier to drive 8 ohm speaker
- ◆ Use special amplifier for this purpose




Lab 2 Task 1 – Half-wave Rectifier

- ◆ Good half-wave rectifier

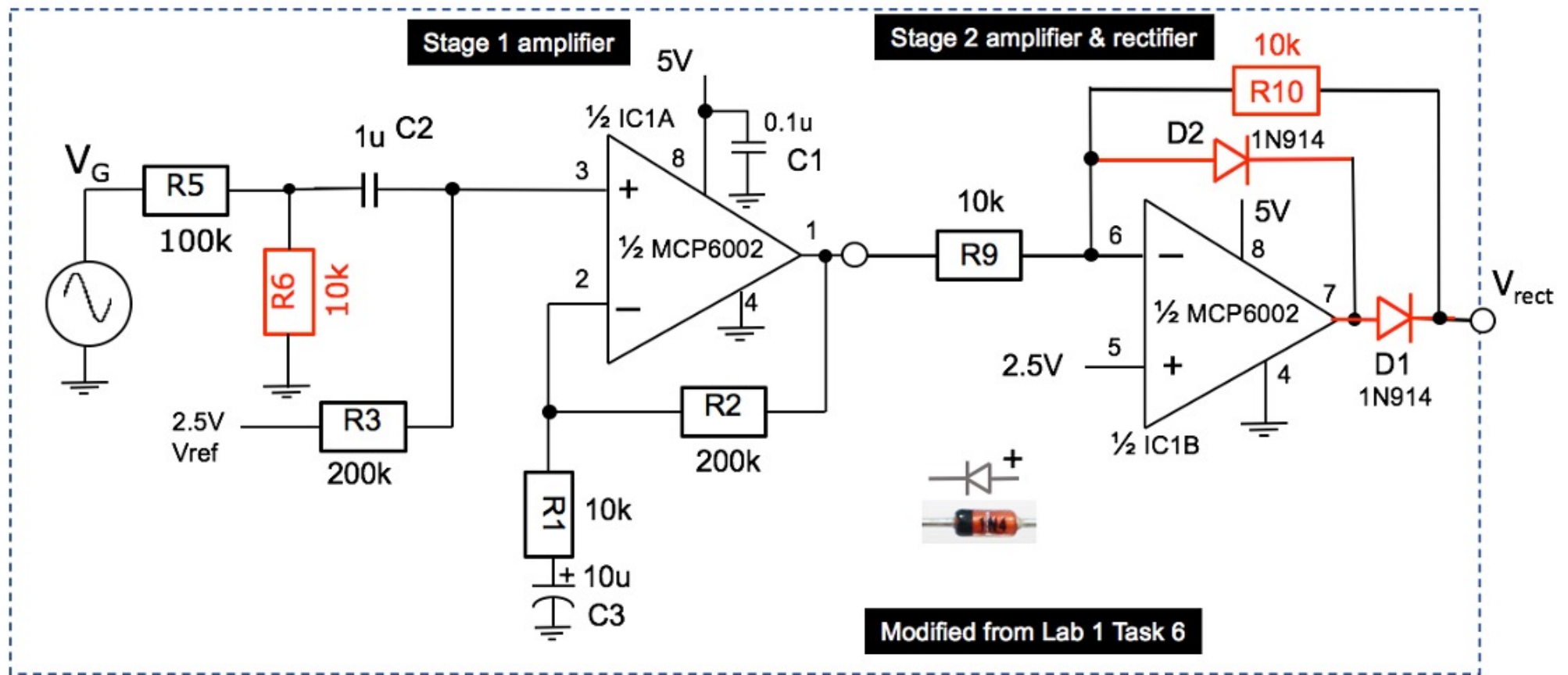


Lab 2 Task 1 – Full-wave rectifier

- ◆ Poor full-wave rectifier

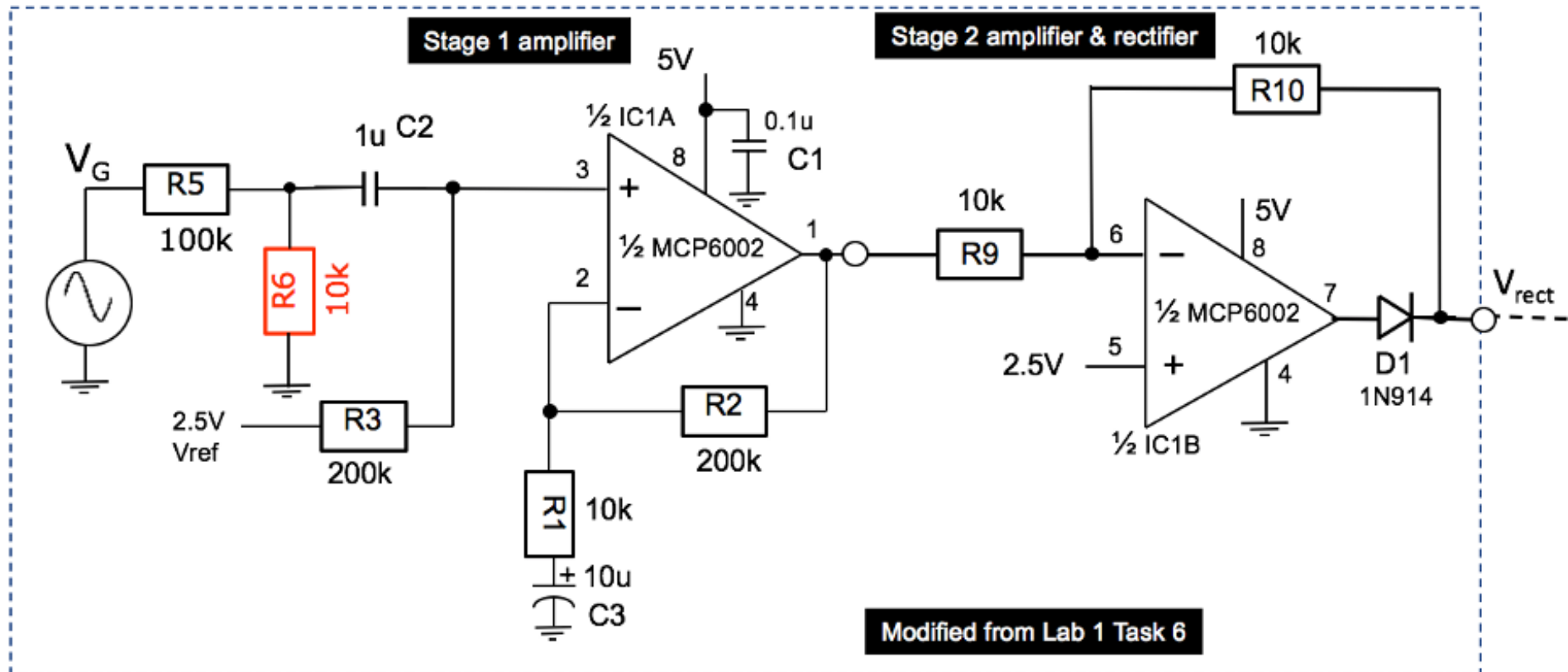


Lab 2 Task 1 – Peak detection

- ◆ Peak detecting

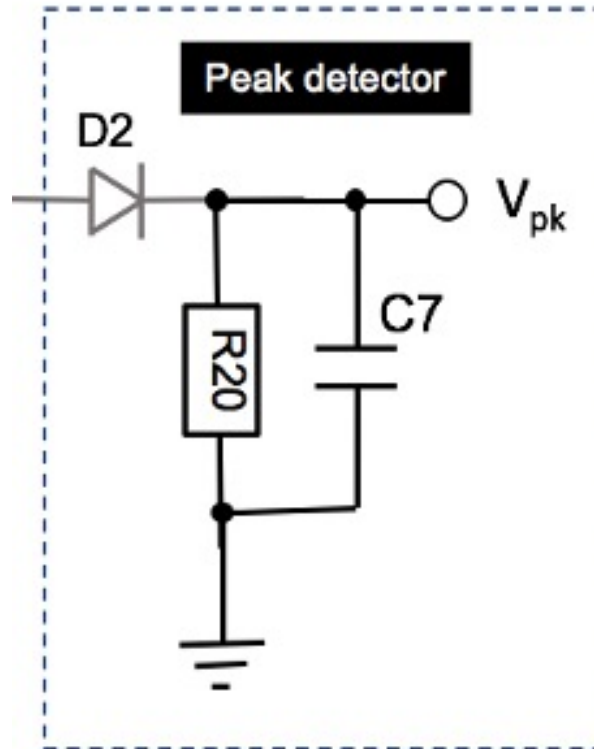


Lab 2 Task 1 – Sound level detection

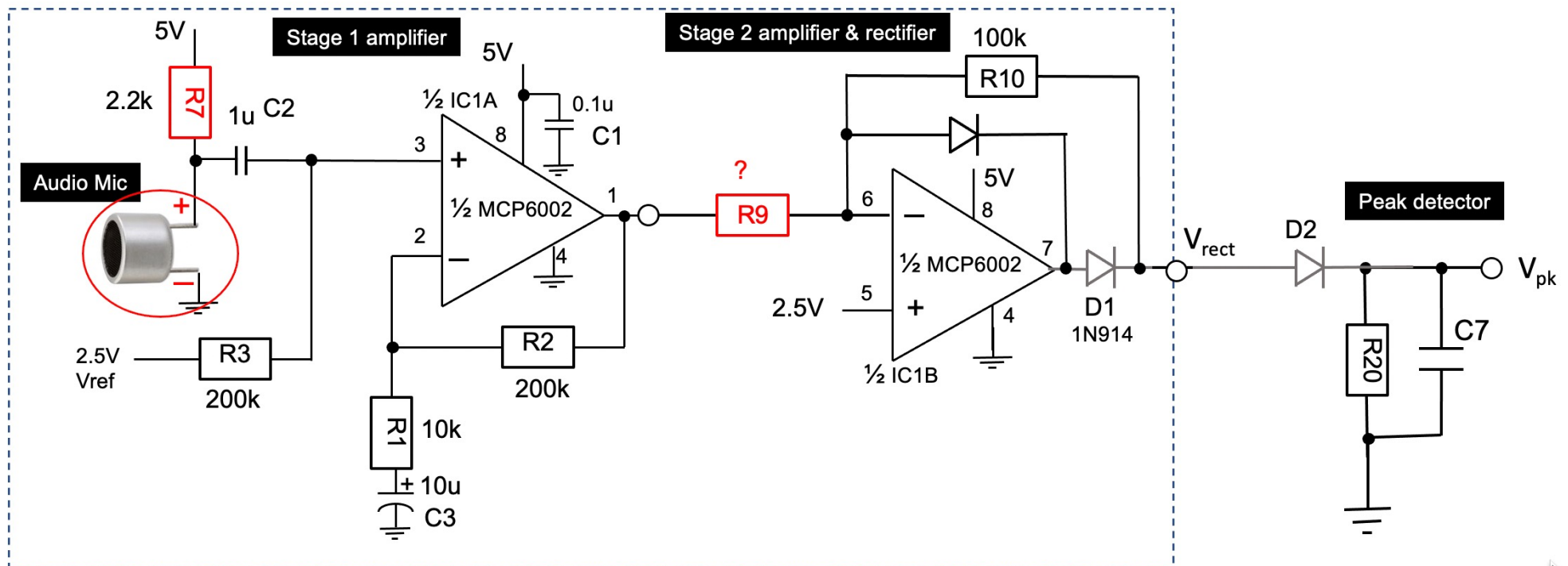
- ◆ R9 – estimate or measure, not easy to calculate



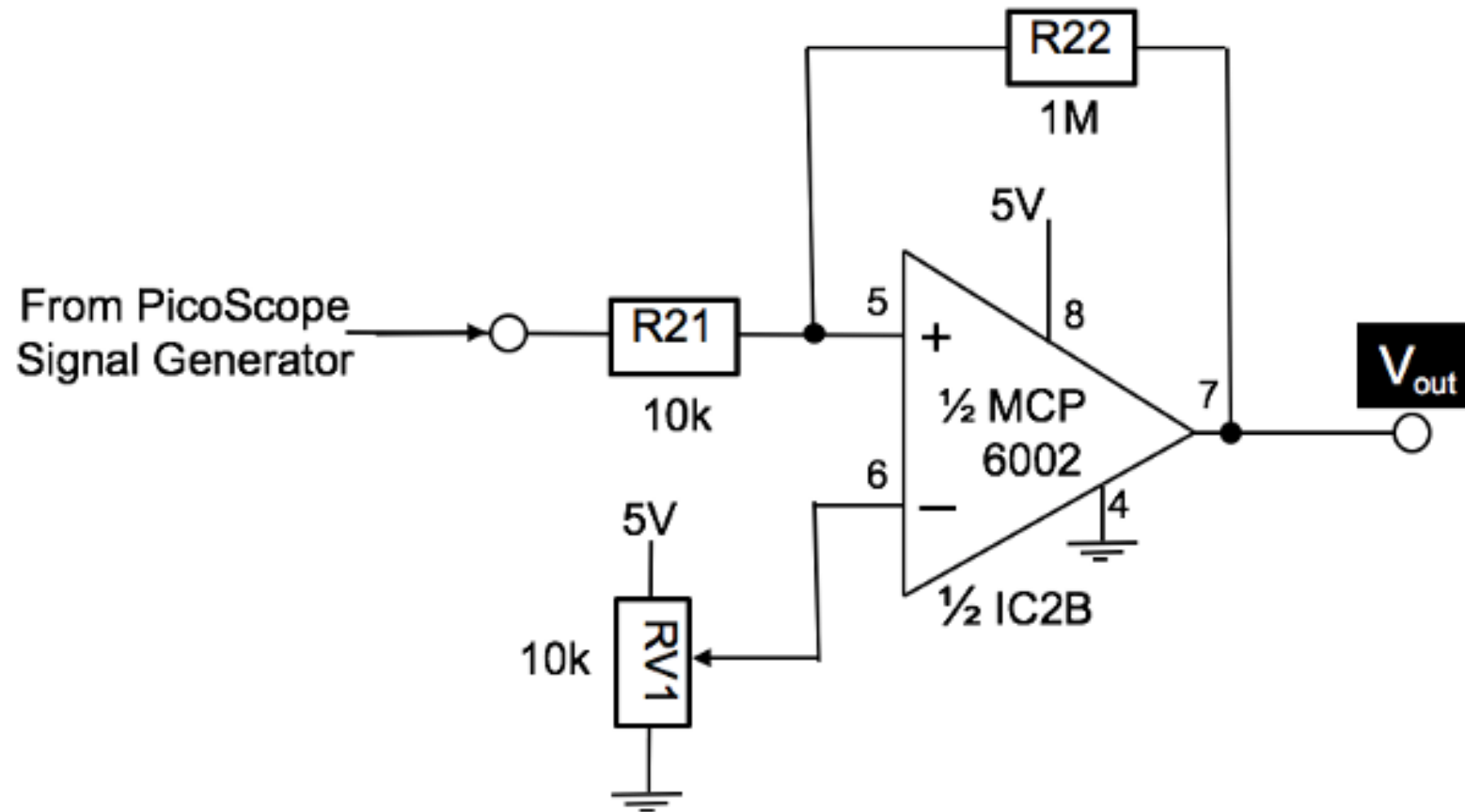
Lab 2 Task 2 – Comparator with hysteresis



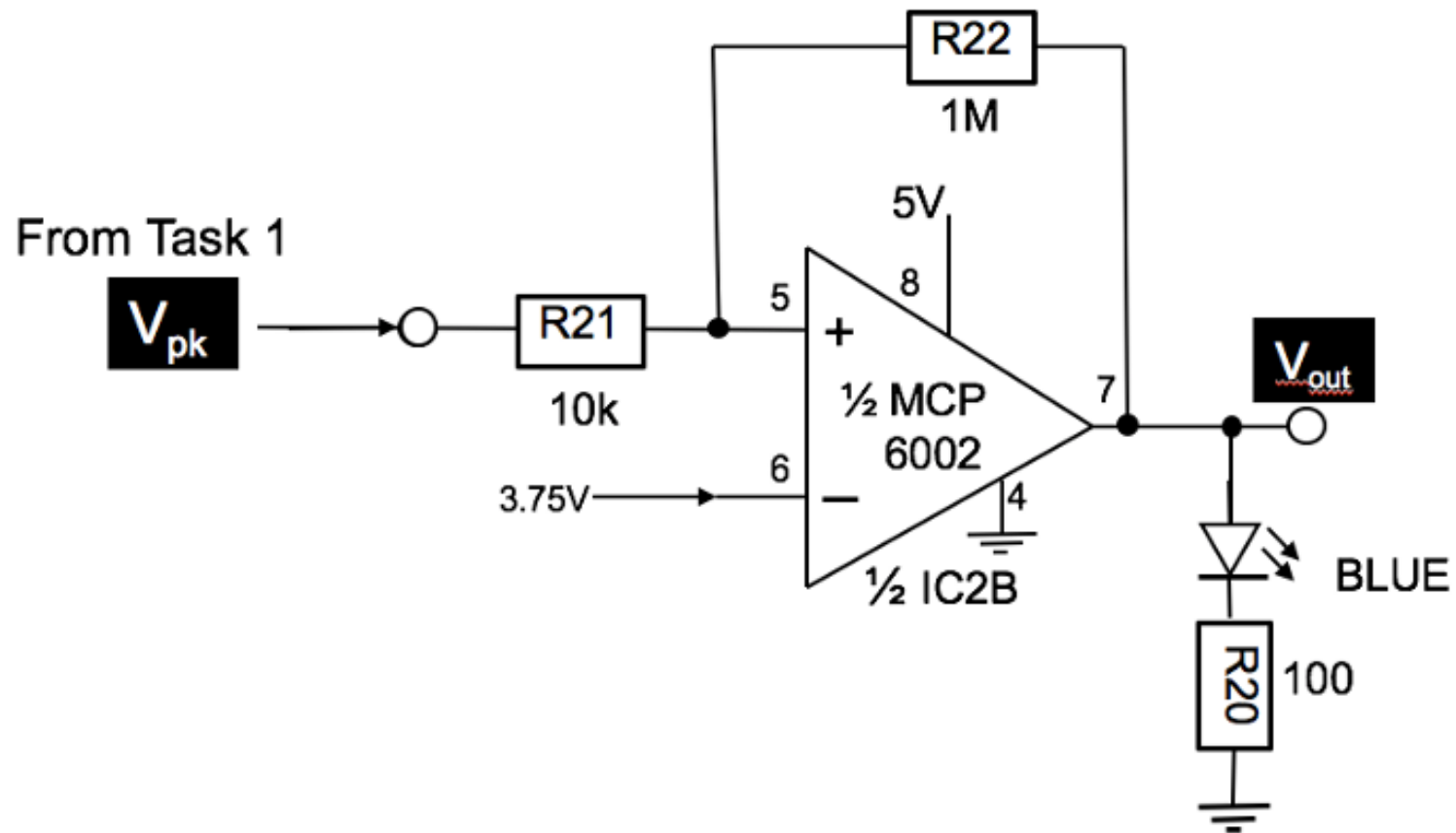
Lab 2 Task 2 – Comparator to detect sound




Lab 2 Task 3 – Function Generator

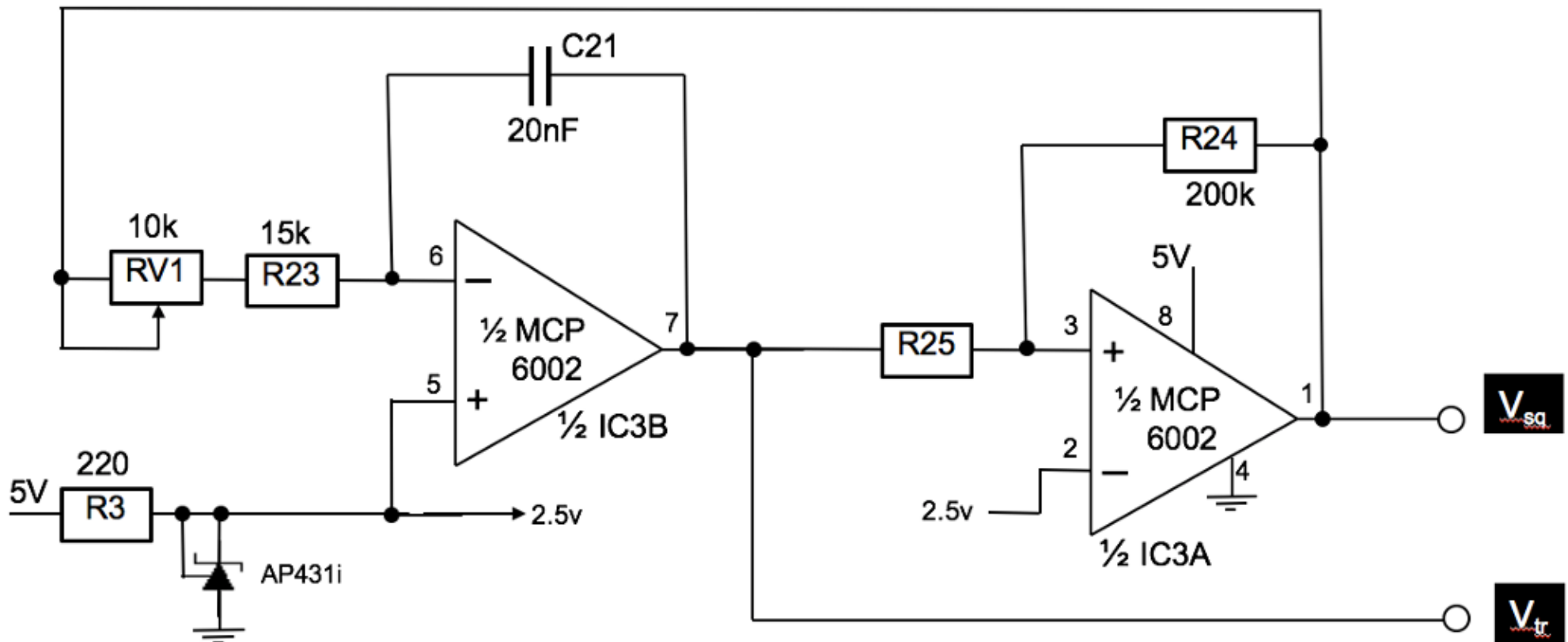

Lab 2 Task 4 – Lowpass filter

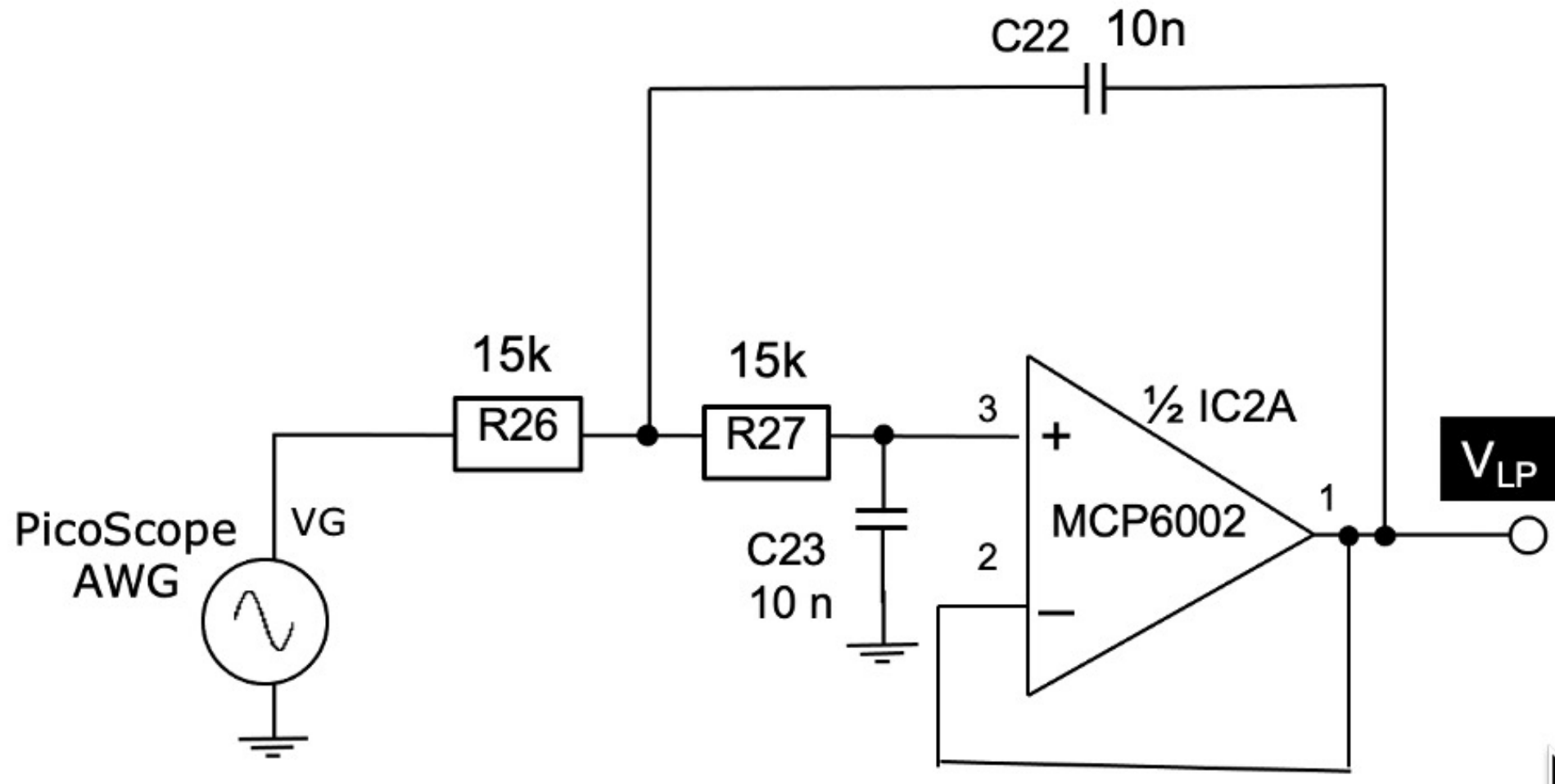

Lab 2 Task 5 – Pulse-width modulator

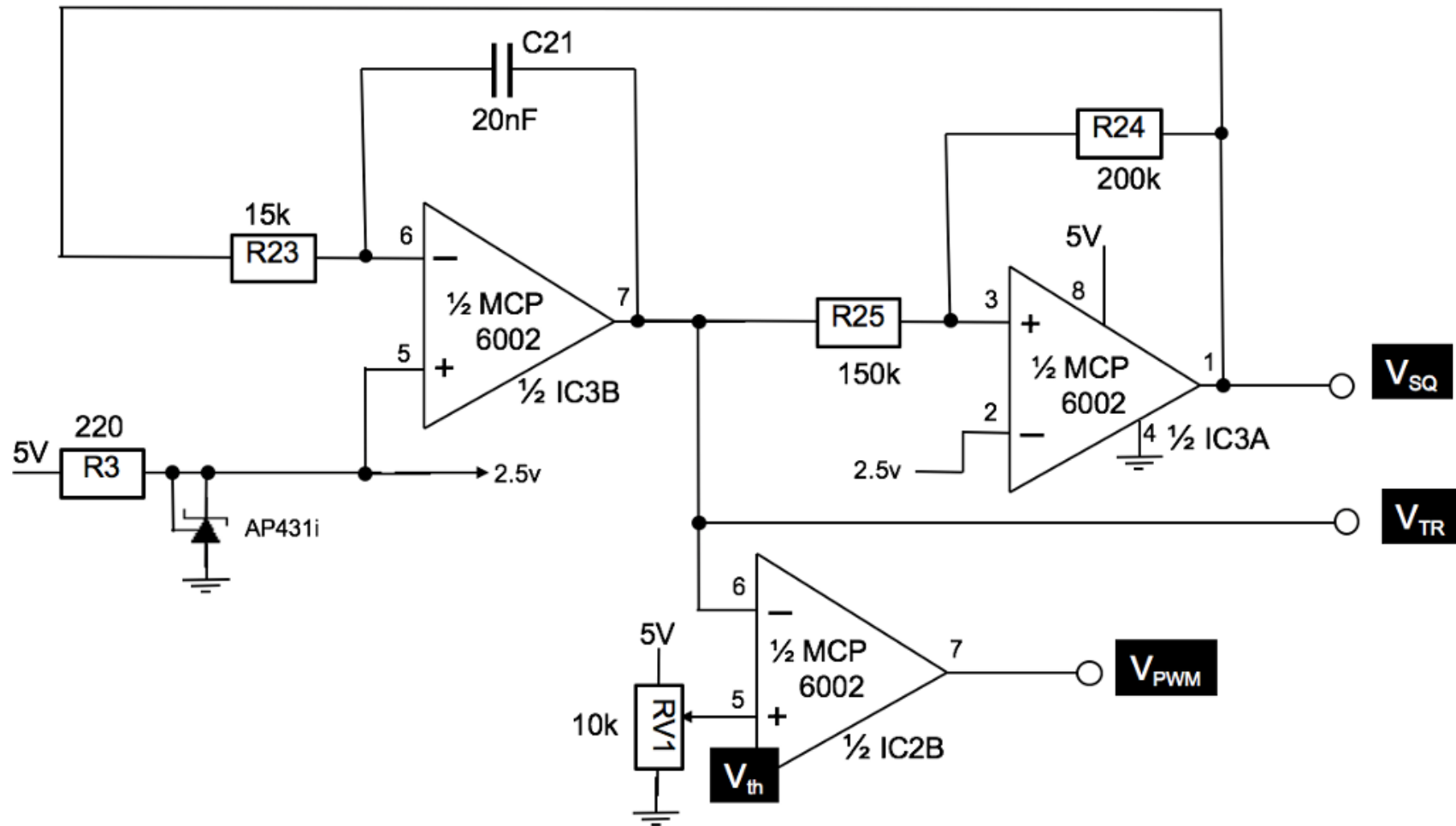

Lab 2 Task 5 – Pulse-width modulator

